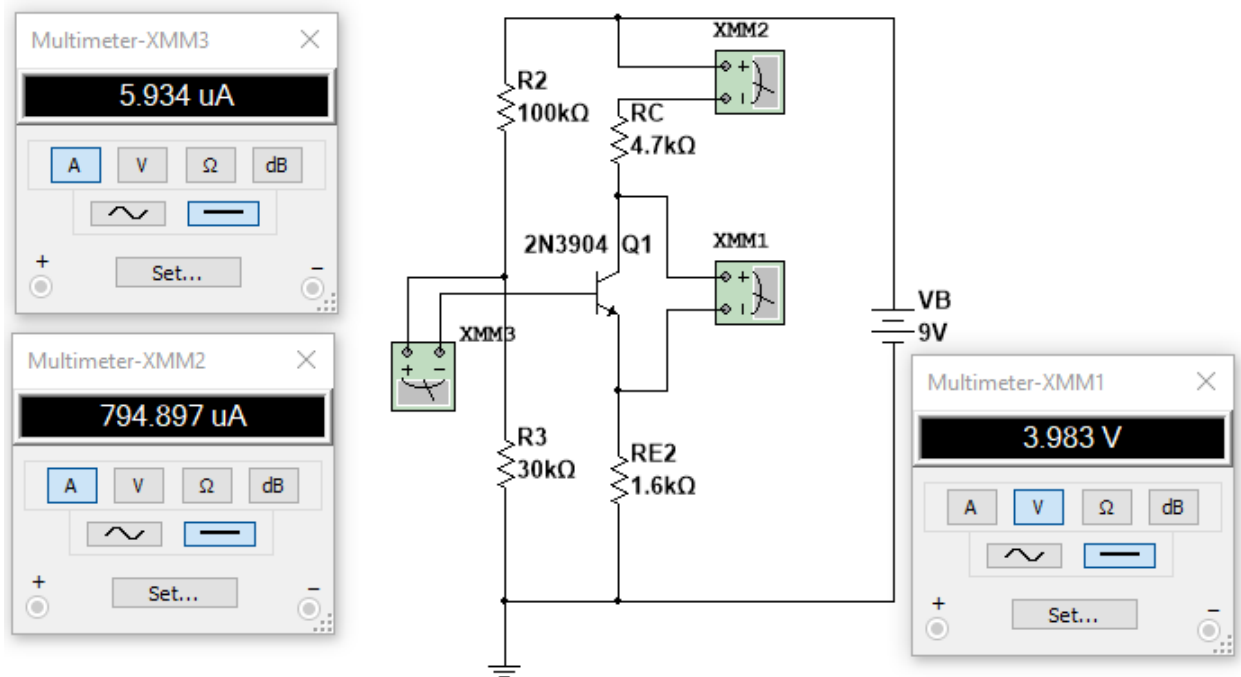


Chapter 3

Common Collector and Common Drain Configurations

1. DC Equivalents and Analysis of these Amplifiers

1.1BJT




Theoretically there is no need to perform the DC analysis since the circuit was kept similar from the DC point of view to the one presented in the case of the common-emitter amplifier

$$\begin{aligned} R2 &= 100\text{e}3; R3 = 30\text{e}3; R_B = 1/(1/R2 + 1/R3); \\ V_{beq} &= 0.7; R_C = 4.7\text{e}3; R_E = 1.6\text{e}3; \\ \beta &= 136; V_B = 9; V_{bb} = R3/(R2 + R3) * V_B; \\ A &= [R_B/\beta + R_E, 0; R_C + R_E, 1]; \\ B &= [V_{bb} - V_{beq}; V_B]; \\ X &= A \setminus B \\ V_{CEQ} &= V_B - (R_C + R_E) * X \\ I_{CQ} &= 778\mu\text{A} \\ V_{CEQ} &= 4.1\text{V} \end{aligned}$$

These numbers are close to the simulated values even though the ratio of the collector current to the base current is approximately 134. We again see how important some parameters are since a small variation of beta (less than 2 %) in a very minor variation of the Q-point. However, if we are facing a 4-fold increase of the beta ratio, there will be noticeable variations of the Q-point if it were not for the presence of R_C .

2.1 MOSFET

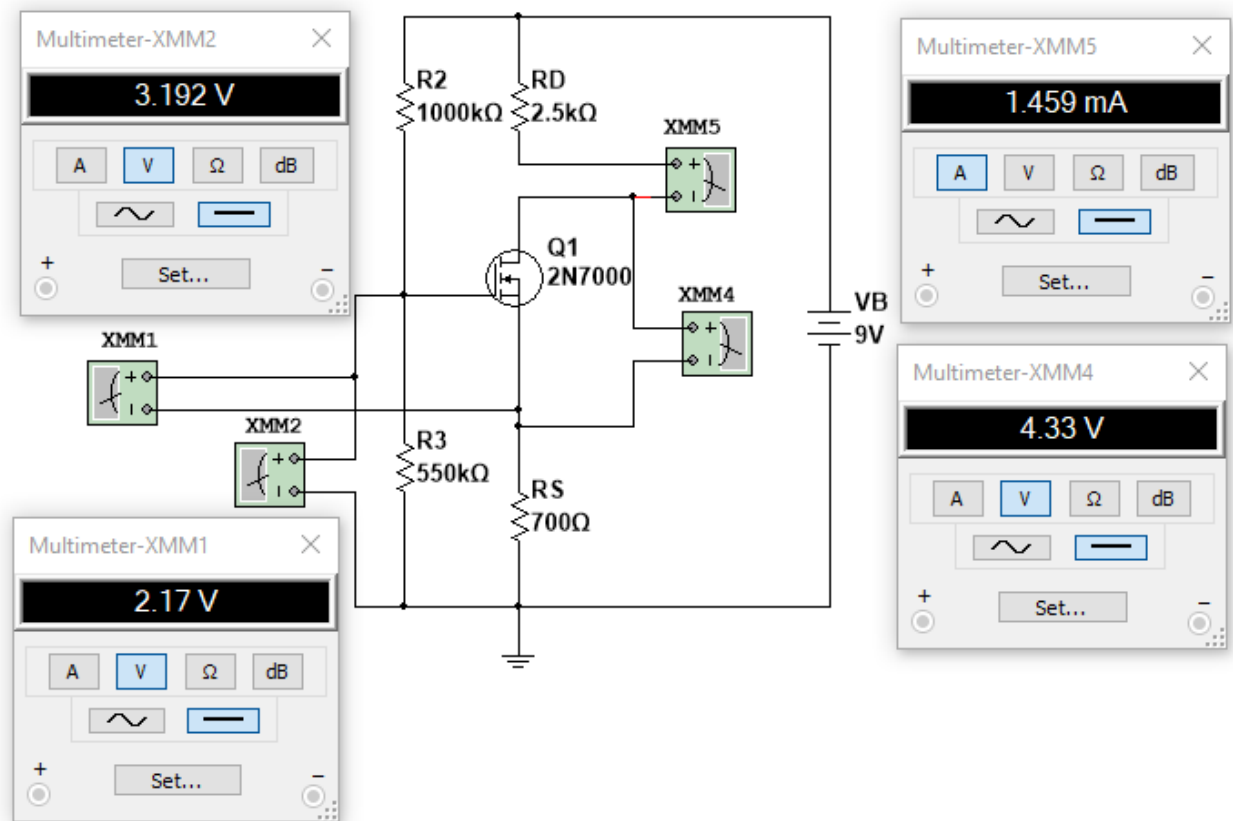

Even though it may not be an optimum choice of the Components values, and the location of the Q-point, we chose the same circuit that was presented as a common-emitter amplifier. Of course, the output will be accessible through the emitter rather than the collector, and the AC performance will be different, but from a DC point of view, the circuit will have the same characteristics. Hence,

$$I_{DS} = 1.46\text{mA}$$

$$V_{DS} = 4.34\text{ V}$$

$$V_{GS} = 2.17\text{V}$$


Since $V_{DS} > V_{GS} - V_{TN} > 0$, the assumption of a saturation region is valid.

These values verify the results obtained in the simulation.

2. AC Analysis

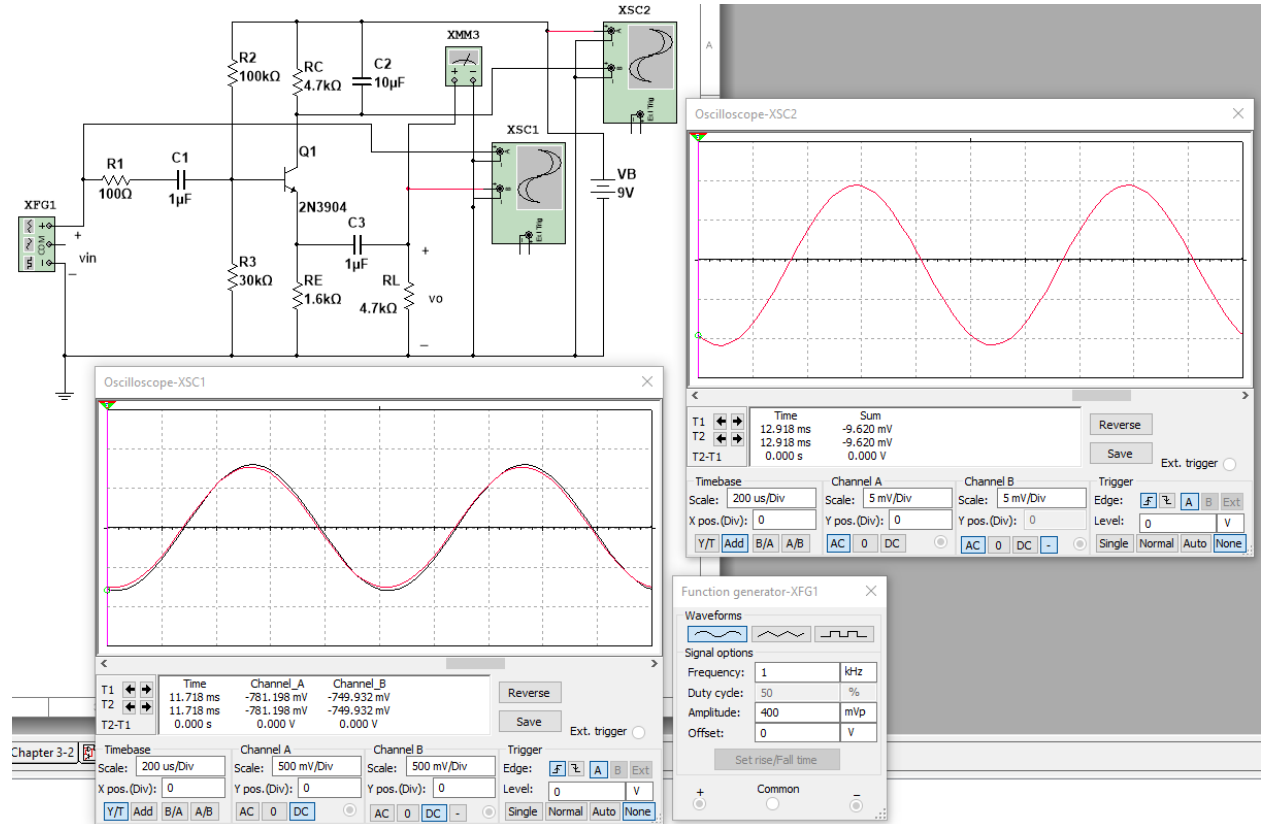
2.1 BJT

The circuit shown below is a common-collector configuration where the output is taken from the emitter, and the input is injected in the path of the base, hence sharing the collector.




Let us assume again that the capacitors have zero impedance at all frequencies except DC. In addition, all the large capacitors in the power supplies will render the DC power supplies into short circuits from an AC point of view.

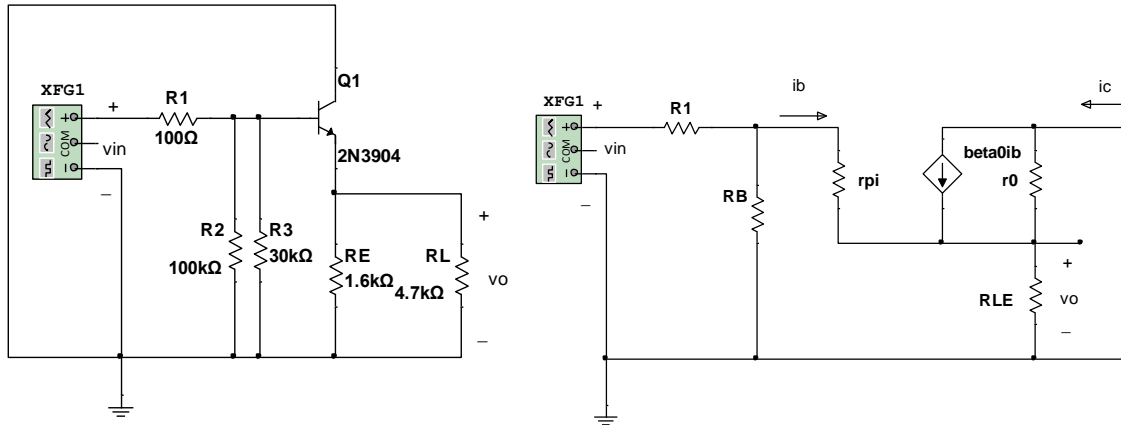The two versions of the AC equivalent are shown below:



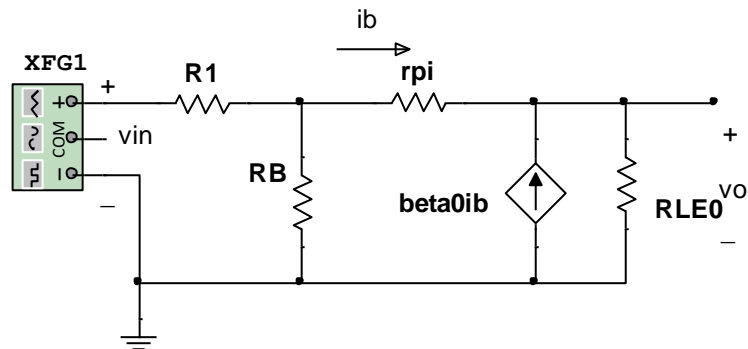2.1.1 Voltage Gain

Let us redraw the last circuit for simpler analysis.



Note that $R_B = R_2 // R_3$, $R_{LE0} = R_L // R_E // r_0$

$$i_b + \beta_0 i_b = \frac{v_0}{R_{LE0}}$$

$$v_b = r_\pi i_b + R_{LE0} (\beta_0 + 1) i_b$$

$$i_b = \frac{v_0}{(\beta_0 + 1) R_{LE0}}$$

$$v_b = (r_\pi + R_{LE0} (\beta_0 + 1)) \frac{v_0}{(\beta_0 + 1) R_{LE0}}$$

$$\frac{v_0}{v_b} = \frac{(\beta_0 + 1) R_{LE0}}{r_\pi + (\beta_0 + 1) R_{LE0}}$$

Since

$$R_{inb} = \frac{v_b}{i_b} = r_\pi + R_{LE0} (\beta_0 + 1)$$

$$\frac{v_b}{v_{in}} = \frac{R_B // R_{inb}}{R_1 + R_B // R_{inb}}$$

$$\frac{v_0}{v_{in}} = \frac{R_B // R_{inb}}{R_1 + R_B // R_{inb}} \frac{(\beta_0 + 1) R_{LE0}}{r_\pi + (\beta_0 + 1) R_{LE0}}$$

Note that the voltage gain is a positive number always less than one. The output signal is in phase with the input signal. This is not an amplifier that amplifies the voltage, however, the current is amplified and therefore there is power amplification. The advantage to using this configuration in the design of a voltage amplifier will be known when we derive the output resistance of a common-collector configuration.

2.1.2 Input Resistance


We have already seen that the input resistance is given by

$$R_{inb} = \frac{v_b}{i_b} = r_\pi + R_{LE0} (\beta_0 + 1)$$

The input resistance is very large.

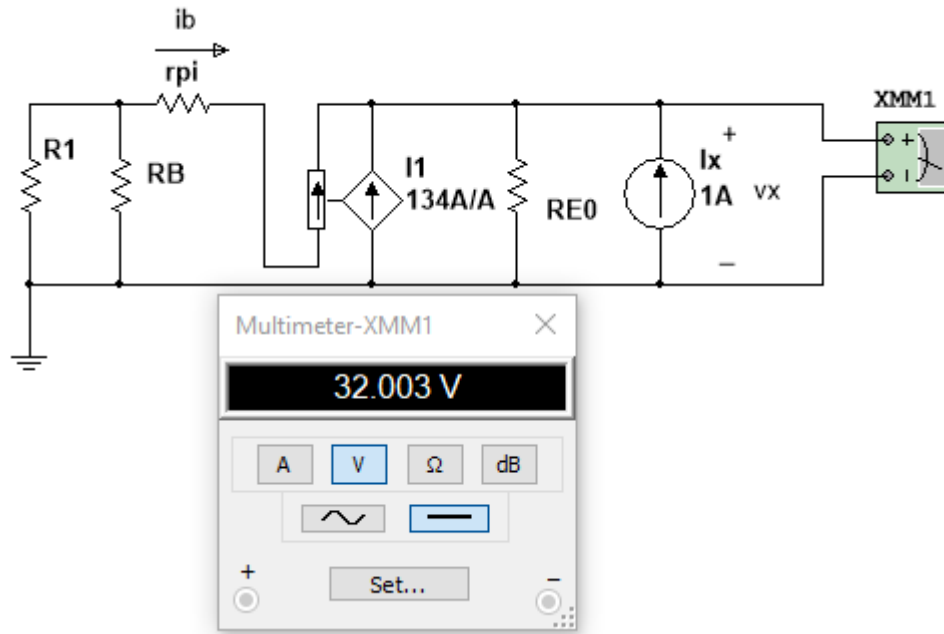2.1.3 Output Resistance

This is the circuit used to evaluate the output resistance seen by the load resistor R_L , where $R_B = R_2 // R_3$, $R_{E0} = R_E // r_0$, and let $R_{th} = R_1 // R_B$.



$$v_x = -(R_{th} + r_\pi)i_b$$

$$v_x = R_{E0}((\beta_0 + 1)i_b + i_x)$$

$$= R_{E0} \left(-(\beta_0 + 1) \frac{v_x}{(R_{th} + r_\pi)} + i_x \right)$$

$$v_x \left(1 + \frac{(\beta_0 + 1)R_{E0}}{(R_{th} + r_\pi)} \right) = R_{E0}i_x$$

$$R_{out} = \frac{v_x}{i_x} = \frac{R_{E0}}{1 + \frac{(\beta_0 + 1)R_{E0}}{(R_{th} + r_\pi)}}$$

If R_{E0} approaches infinity (equivalent to looking directly into the emitter)

$$R_{out} = \frac{R_{th} + r_\pi}{\beta_0 + 1}$$

and if $\beta_0 \gg 1$

$$R_{out} = \frac{R_{th} + r_\pi}{\beta_0}$$

$$R_{out} = \frac{1}{g_m} + \frac{R_{th}}{\beta_0}$$

```

R1=100;R2=100e3;R3=30e3;RC=4.7e3;RL=4.7e3;RE=1.6e3;
RB=1/(1/R2+1/R3);RLE=1/(1/RL+1/RE);beta=134;
VB=9;VBB=R3/(R2+R3)*VB;Rth=1/(1/R1+1/RB);
ICQ=778e-6;VCEQ=4.1;VA=74.03;
gm=40*ICQ; rpi=beta/gm; r0=(VA+VCEQ)/ICQ;
RLE0=1/(1/RL+1/RE+1/r0);
Rinb=rpi+RLE0*(1+beta);
RinbB=1/(1/RB+1/Rinb);
Gain=RLE0*(1+beta)/(rpi+RLE0*(1+beta))*RinbB/(R1+RinbB);
Rin=R1+RinbB;
Rout=(Rth+rpi)/(beta+1);
disp(['The exact voltage gain is ',num2str(Gain)])
%disp(['The voltage gain (first approximation) is ',num2str(Gain1)])
disp(['The input resistance is ',num2str(Rin/1000),' kOhms'])
disp(['The output resistance seen by RL is ',num2str(Rout),' Ohms'])

```

The exact voltage gain is 0.96888


The input resistance is 20.3235 kOhms

The output resistance seen by RL is 32.6332 Ohms


The input resistance could be increased by increasing R_2 and R_3 while maintaining the same Q-point. Note that there is also less AC power dissipation by using a capacitor across R_C while limiting the frequency response.

	Calculated	Simulated	Error %
Voltage Gain	0.969	0.958	0.64
R_{in}	20.324k Ω	354.46k Ω *	0.14
R_{iE}	164.7k Ω	164.69k Ω	0.006
R_{out}	32.63 Ω	32.003 Ω	0

2.2 MOSFET

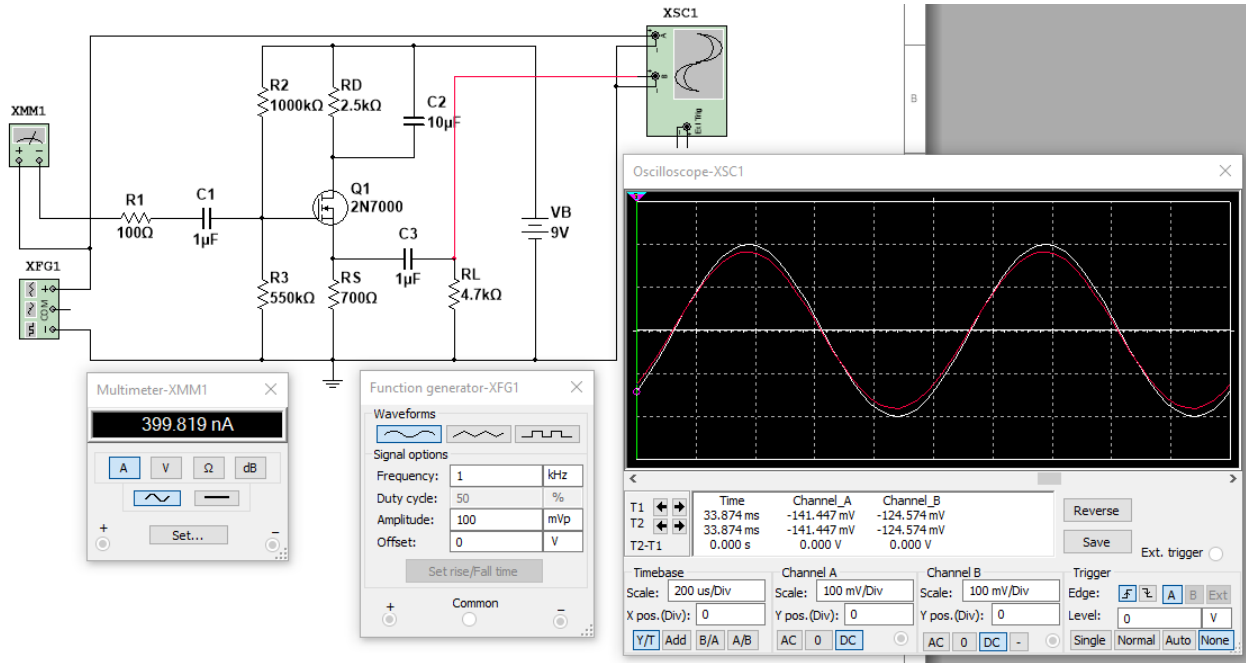

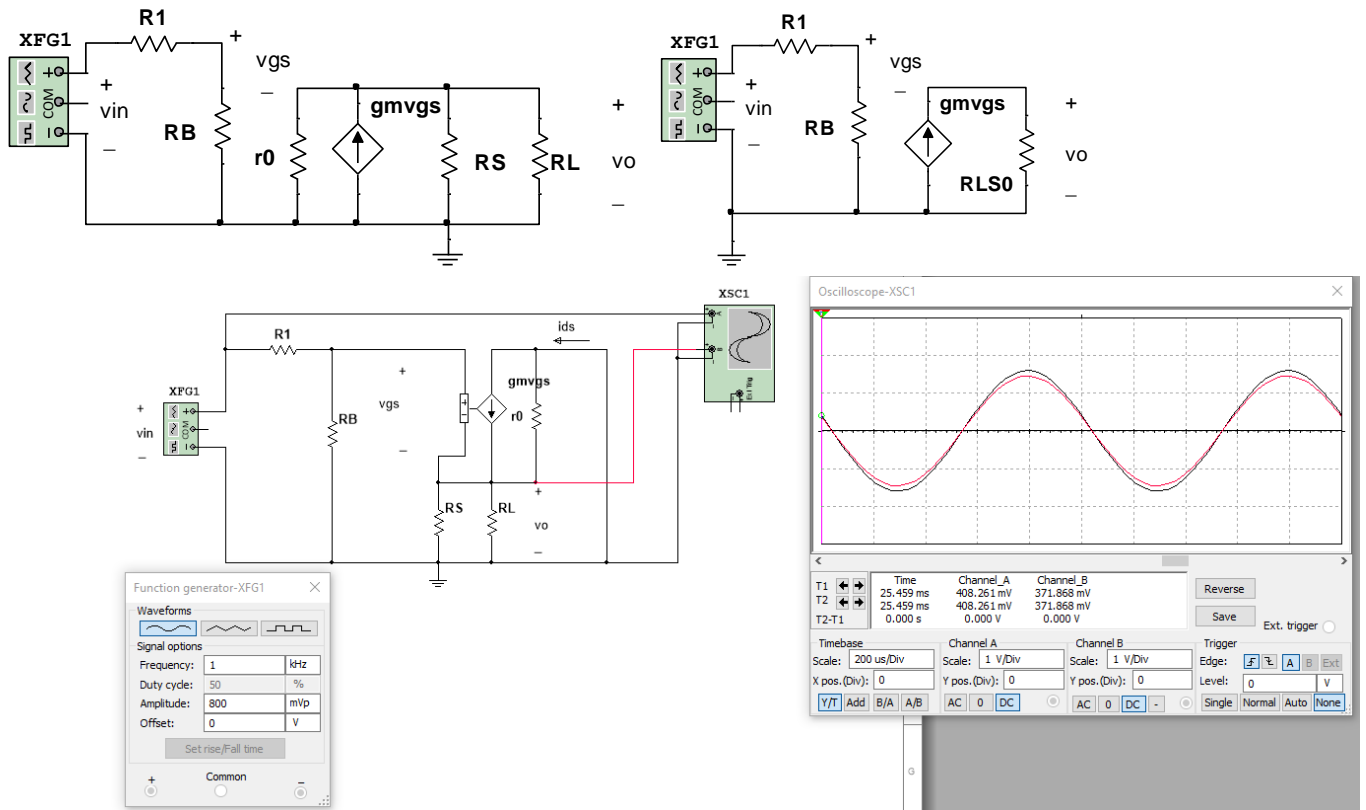The two circuits shown below are the AC equivalent of the MOSFET-based circuit.



Note that $R_B = R_2 // R_3$, $R_{LS0} = R_L // R_S // r_o$

2.2.1 Voltage Gain

$$-v_g + v_{gs} + v_o = 0$$

$$v_o = g_m v_{gs} R_{LS0}$$

$$-v_g + \frac{v_o}{g_m R_{LS0}} + v_o = 0$$

$$\frac{v_o}{v_g} = \frac{g_m R_{LS0}}{1 + g_m R_{LS0}}$$

Since

$$\frac{v_g}{v_{in}} = \frac{R_B}{R_1 + R_B}$$

$$\frac{v_o}{v_{in}} = \frac{R_B}{R_1 + R_B} \frac{g_m R_{LS0}}{1 + g_m R_{LS0}}$$


2.2.2 Input Resistance

The input resistance seen by the voltage source v_{in} is

$$R_{in} = R_1 + R_B$$

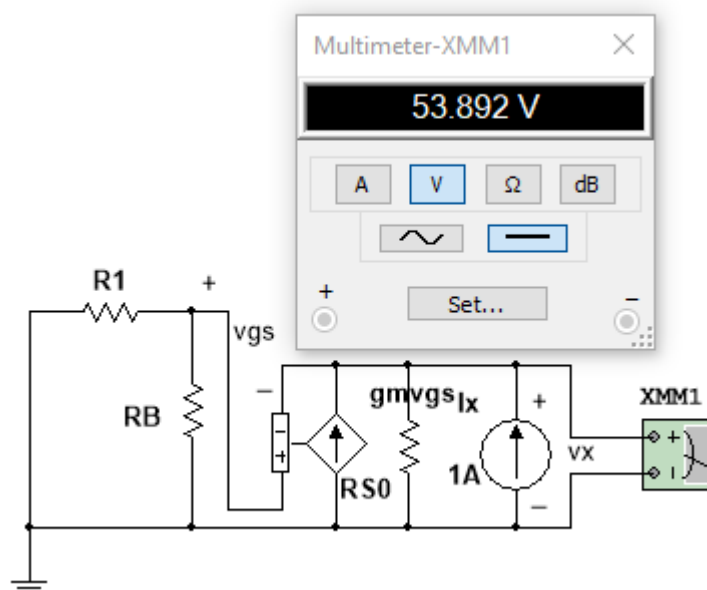2.2.3 Output Resistance

The output resistance seen by R_L is derived as follows:



$$+v_{gs} + v_x = 0$$

$$v_x = (i_x + g_m v_{gs}) R_{s0}$$

$$v_x = (i_x - g_m v_x) R_{s0}$$

$$v_x (1 + g_m R_{s0}) = i_x R_{s0}$$

$$R_{out} = \frac{v_x}{i_x} = \frac{R_{s0}}{(1 + g_m R_{s0})}$$

$$R_{out} = \frac{1}{g_m} // R_{s0}$$

$$R_{iS} = \frac{1}{g_m}, \text{ resistance seen looking into the source}$$

```

R1=100;R2=1000e3;R3=550e3;RD=2.5e3;RL=4.7e3;RS=700;Kn=0.1;
RG=1/(1/R2+1/R3);
VB=9;VG=R3/(R2+R3)*VB;Rth=1/(1/R1+1/RG);
IDSQ=1.46E-3;VDSQ=4.34;lambda=1/50;
gm=sqrt(2*Kn*IDSQ);r0=(1/lambda+VDSQ)/IDSQ;
RiS=1/gm;RS0=1/(1/RS+1/r0);RLS0=1/(1/RS0+1/RL);
Gain=gm*RLS0/(1+gm*RLS0);
Rin=R1+RG;
Rout=1/(1/RS0+1/RiS);
disp(['The exact voltage gain is ',num2str(Gain)])
disp(['The input resistance is ',num2str(Rin/1000),' kOhms'])
disp(['The output resistance seen from the emitter is ',num2str(RiS),' Ohms'])
disp(['The output resistance seen by RL is ',num2str(Rout),' Ohms'])

```

The exact voltage gain is 0.91106

The input resistance is 354.9387 kOhms

The output resistance seen from the emitter is 58.5206 Ohms

The output resistance seen by RL is 53.9274 Ohms


	Calculated	Simulated	Error %
Voltage Gain	0.91106	0.911	0
R_{in}	354.94k Ω	354.94k Ω	0
R_{iS}	58.52 Ω	58.48 Ω	0.07
R_{out}	53.93 Ω	53.9 Ω	0.06

Note that the simulation showed that even a 1.6 Vp input sinewave exhibited no distortion visible to the naked eye, verifying that a MOSFET has a much wider input signal range. Its much wider signal range makes it a stage required to process the amplified version of a signal without distortion.

The output resistance is much lower than the output resistance of a common-source amplifier, making it the desired last stage needed to design a voltage amplifier.

3. Input Signal Range

3.1 BJT

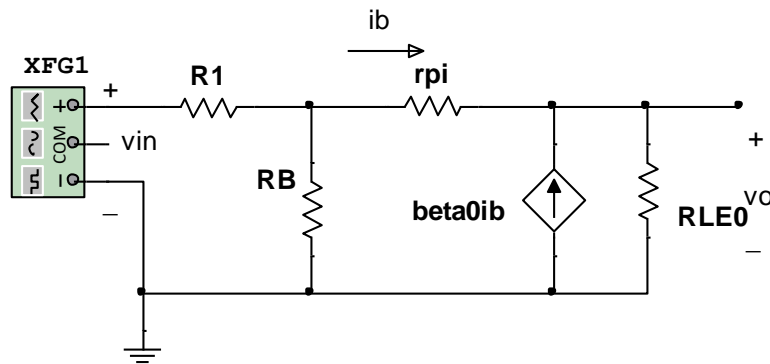

$$v_b = r_{\pi} i_b + (\beta_0 + 1) i_b R_{LE0}$$

Since $r_{\pi} i_b = v_{be}$

$$v_b = v_{be} + (\beta_0 + 1) \frac{v_{be}}{r_{\pi}} R_{LE0}$$


$$v_b = v_{be} \left(1 + \frac{\beta_0 + 1}{r_{\pi}} R_{LE0} \right)$$

$$v_b \leq 0.005 \left(1 + \frac{\beta_0 + 1}{r_{\pi}} R_{LE0} \right)$$

and if $\beta_0 \gg 1$

$$v_b \leq 0.005(1 + g_m)R_{LE0}$$

3.2 MOSFET

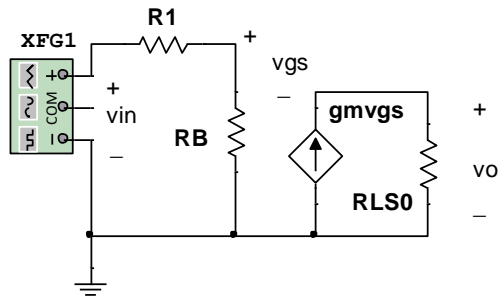

$$v_g = v_{gs} + g_m v_{gs} R_{LS0}$$

$$v_g = v_{gs} (1 + g_m R_{LS0})$$

$$v_g \leq 0.2(V_{GS} - V_{TN})(1 + g_m R_{LS0})$$

We see now that the two most important advantages of having an emitter or a source resistor, aside from a better control over the Q-point, are an increased input resistance, and an increased input signal range.